





Light control: innovate, more silent magnetic relay.

Its patented technology certified by the **University of Turin** works by utilising simple magnetic and electrical components.



Relay with 2 sequential outputs



Sequential relay with reset push button



Sequential relay with 3 terminals



Sequential relay with 4 terminals

It is flexible

In the new version with 4 terminals, the push button to control the load can be wired with both phase and with neutral. It can replace traditional relays regardless of the type of connection.



It is more silent.

Unlike electromechanical devices, the change of status proves **more silent**.



QUID offers the possibility of creating a **centralised power-off** control also in traditional systems. Used to turn off all the lights with a single gesture, it is also ideal in hotel rooms, associated with the headboard device, or at the entrance to a home.



It is safe and efficient.

Even if the push button remains active, the relay **does not overheat** because the current is not present after the change of status. Its stability and outstanding operation has been certified by the Physics Department at the University of Turin.









Roller shutter control: reliable and safe switch for centralised operation.

Innovative and reliable, it supports advanced functions even on wired systems: offering you the chance to automate curtains or roller shutters by enabling their control in groups, with load cut-off at the limit stop and saving of the favourite position.











Eikon

Linea

Arké

Offers coordinated centralised operation.

A top-performing solution devised to ensure functionality and comfort.

It is aware of the surrounding occupants' habits.

It saves your favourite curtain and roller shutter positions. The user can call it up at any time at the touch of a finger.



It is reliable and safe.


It cuts off the voltage at the limit stop to avoid the motor remaining under voltage and being damaged.




quid+

Typical systems - Lights

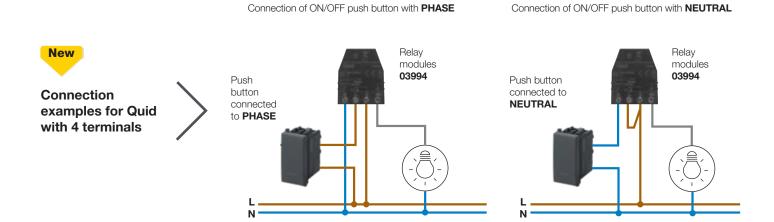Connection examples with Quid magnetic relay module for controlling lights.



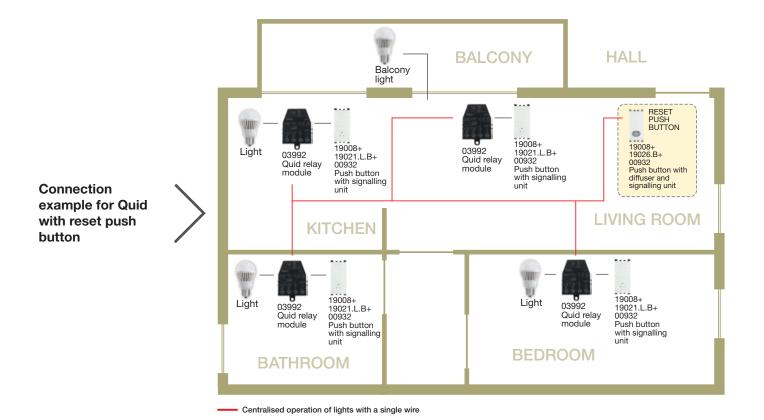Connection example for Quid with 3 terminals



Relays for lights

Relay with sequential ON/OFF pulses, with wiring on phase (L) or neutral (N)

03994 Magnetic Quid relay module with sequential ON/OFF pulses, 1 input for NO pu

Magnetic Quid relay module with sequential ON/OFF pulses, 1 input for NO push button on phase (L) or on neutral (N), 1 NO 10 AX 220-240 V~ 50/60 Hz relay output, flush mounting (retrofit, shunting or under blank module) - Depth: 22.5 mm







Relay with sequential ON/OFF pulses

Magnetic relay module with sequential ON/OFF pulses, 1 input for NO push button, 1x10 A 220-240 V~ 50/60 Hz relay output, installation in junction boxes or connector block boxes - Depth: 22.5 mm





Relay with sequential ON/OFF pulses, with input for reset push button

Magnetic relay module with sequential ON/OFF pulses, 1 input for NO push button, 1 input for reset push button, 1x10 A relay output, 220-240 V~ 50/60 Hz power supply, light signal for the load status on each individual push button, installation in junction boxes or connector block boxes - Depth: 22.5 mm





Relay with sequential ON/OFF pulses and 2 sequential outputs

Magnetic relay module with sequential ON/OFF pulses, 1 input for NO push button, 2x10 A sequential relay outputs, 220-240 V~ 50/60 Hz power supply, installation in junction boxes or connector block boxes - Depth: 23 mm





03993

Pre-wired LED signalling unit

Pre-wired load status LED signalling unit, for Quid pulse relay module with pulse control push buttons 03992, 220-240 V 50/60 Hz 0.5 W power supply, green

00945.G LED signalling unit for aligned and axial controls, for front insertion under the button, for Quid pulse relay module with pulse control push buttons 03992, green





0093

Relays for roller shutters

Electronic switch for roller shutter


Electronic switch for roller shutter with slat orientation with relay outputs for cos 0.6 motor 2 A 220-240 V~ 50/60 Hz, position saving - Depth: 41.5 mm (Eikon and Linea), 40.5 mm (Arké and Plana).

EIKON







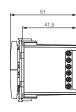


LINEA





30196.C

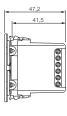


ARKÉ








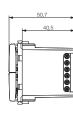

PLANA





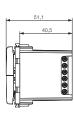

Retrofit electronic relay module for roller shutter

03996

Electronic relay module for roller shutter with slat orientation with relay outputs for cos¢ 0.6 motor 2 A 220-240 V~ 50/60 Hz, position saving, installation in junction boxes or connector block boxes - Depth: 22.5 mm





Roller shutter control unit module

03997

Roller shutter control unit module, 2 inputs for NO push button, 6 outputs for Quid roller shutter relay module 03996, 220-240 V 50/60 Hz power supply, installation in junction boxes or connector block boxes - Depth: 22.5 mm









Typical systems - Roller shutters

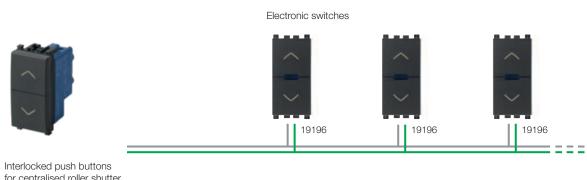Example with Quid electronic switches for roller shutter control and devices for centralised control.



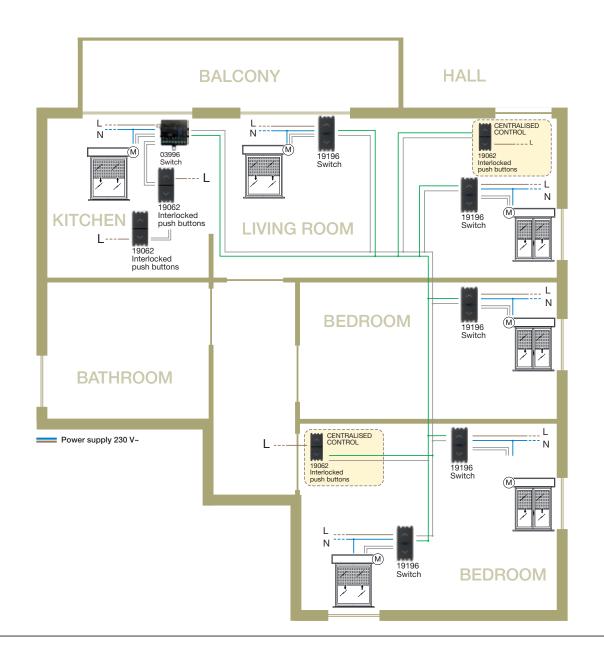Interlocked push buttons for centralised roller shutter opening/closing (19062).



5 EN 2407

Energia Positiva. Insieme

